

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)
ORGANISATION OF ISLAMIC COOPERATION (OIC)
Department of Computer Science and Engineering (CSE)

MID SEMESTER EXAMINATION

SUMMER SEMESTER, 2021-2022

DURATION: 1 HOUR 30 MINUTES

FULL MARKS: 75

CSE 4205: Digital Logic Design

Programmable calculators are not allowed. Do not write anything on the question paper.

Answer **all 3 (three)** questions. Figures in the right margin indicate full marks of questions whereas corresponding CO and PO are written within parentheses.

1. \sqrt{a} Convert the following numbers to the designated bases: 2 × 5
 - i. $(40.876)_{10} = (?)_2$ (CO1)
 - iii. $(124425)_9 = (?)_3$ (PO1)
 - ii. $(ABBA.AC)_{16} = (?)_8$ (CO1)
 - iv. $(CACCA)_{16} = (?)_4$ (PO1)
 - v. $(123.123)_{10} = (?)_2$ (CO1)

The answer should contain the intermediate steps for the calculation of the conversion.
- \sqrt{b} Answer the following questions: 5 × 3
 - i. Draw the block diagram of a digital computer. (CO1)
 - ii. Prove the following Boolean equation using the truth table: $AB + ABC = AB$. (PO1)
 - iii. The formal definition of Boolean Algebra follows Huntington's postulates. These postulates are arranged in pairs. Describe the property for which the postulates are listed in pairs.
2. \sqrt{a} Write down the Boolean expression for the following logic operations: 1 × 5
 - i. x/y (CO1)
 - ii. $x \oplus y$ (PO1)
 - iii. $x \downarrow y$ (CO1)
 - iv. $x \subset y$ (PO1)
 - v. $(x \oplus y)'$ (CO1)
- \sqrt{b} A majority gate is a digital circuit whose output is equal to 1 if the majority of the inputs are 1's. The output is 0 otherwise. By means of a truth table, find the Boolean function implemented by a 3-input majority gate. Simplify the function. 9 (CO2) (PO2)
- \sqrt{c} Design a combinational circuit that detects an error in the representation of a decimal digit in BCD. In other words, obtain a logic diagram whose output is logic-1 when the inputs contain an unused combination in the code. Use the fundamental gates to show the logic diagram. 9 (CO2) (PO2)
- \sqrt{d} Using the block diagram method, convert the solution logic diagram of question 2.c) to NAND implementation and NOR implementations. 2 (CO1) (PO1)
3. \sqrt{a} Simplify the Boolean expression using K-map and show it in SOP form for 12

$$F(p, q, r, s, t) = \prod(1, 3, 5, 7, 9, 11, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31)$$
(CO1) (PO1)
- \sqrt{b} Design a combinational circuit that converts a decimal digit from 8,4,-2,-1 code to BCD. 13 (CO2) (PO2)